

# Frequency Response

Prelab 10

Spring 2021

## 1 Purpose

Find the analytical expression for magnitude and phase of a transfer function.

## 2 Deliverables Overview

- Typed and properly formatted derivation for both the magnitude and phase of the transfer function. *Note: All steps must be shown.*

## 3 Part 1

### 3.1 Tasks

Consider the RLC circuit in figure 1.

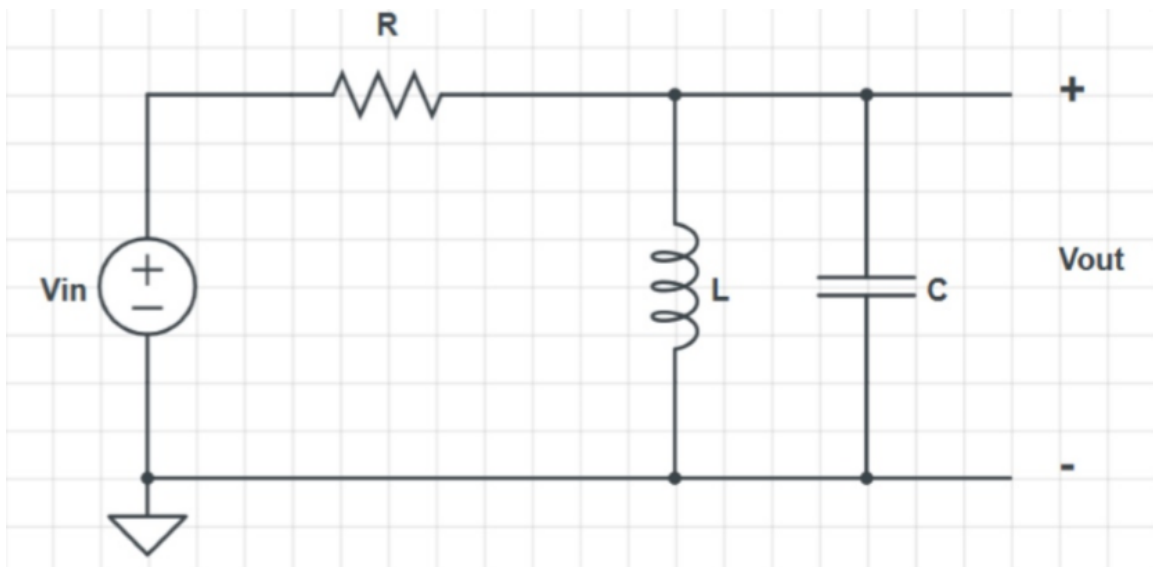


Figure 1:  $R = 1 \text{ k}\Omega$ ,  $L = 27 \text{ mH}$ ,  $C = 100 \text{ nF}$

Which has the transfer function,

$$H(s) = \frac{\frac{1}{RC}s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}.$$

1. By hand, find the magnitude  $|H(j\omega)|$  and the phase  $\angle H(j\omega)$  for the RLC transfer function  $H(s)$ . Type the analytical derivation symbolically in terms of R, L, and C. Do not use your calculator or Python on this step, show all your work.

$$H(j\omega) = \frac{\frac{1}{RC} j\omega}{(j\omega)^2 + \frac{1}{RC} j\omega + \frac{1}{LC}} = \frac{\frac{1}{RC} j\omega}{\frac{1}{RC} j\omega + \left(\frac{1}{LC} - \omega^2\right)} = \frac{j\omega}{RC(LCj\omega + RC - RL\omega^2)} = \frac{j\omega}{RC^2(Lj\omega + R - RL\omega^2)}$$

$$|H(j\omega)| = \frac{\omega}{RC^2 \sqrt{(R - RL\omega^2)^2 + (L\omega)^2}} = \frac{\omega}{RC^2 \sqrt{R^2 - 2R^2L\omega^2 + R^2L^2\omega^4}} = \frac{\omega}{RC^2 \sqrt{1 - 2LC\omega^2 + L^2C^2\omega^4}}$$

$$|H(j\omega)| = \frac{\omega}{RC^2 \sqrt{1 - 2LC\omega^2 + L^2C^2\omega^4}}$$

$$\angle H(j\omega) = \frac{\pi/2}{\tan^{-1} \left[ \frac{RC^2}{RC^2} \frac{L\omega}{R - RL\omega^2} \right]}$$

$$\angle H(j\omega) = \frac{\pi}{2 \cdot \tan^{-1} \left( \frac{L\omega}{R(1 - LC\omega^2)} \right)}$$

