

$$\text{Mag @ } \omega_c \text{ is } -3 \text{ dB} = -0.707$$

as for range 1.8 kHz to 2 kHz
attenuation must be no more than
-0.3 dB. Thus, cut-off frequencies
must be selected to fit this range.

Choose cut-off of 1.2 kHz & 2.6 kHz.

$$\omega_{c1} = 1.2 \text{ kHz} ; \omega_{c2} = 2.6 \text{ kHz}$$

$$\omega_0 = 1.9 \cdot 2\pi \cdot 10^3 \frac{\text{rad}}{\text{s}}$$

$$\omega_0 = \sqrt{\frac{1}{LC}} \Rightarrow LC = \frac{1}{\omega_0^2} = 7.017 \text{ nHF}$$

$$LC = 277 \cdot 10^{-9} \Rightarrow L = \frac{7.017 \cdot 10^{-9}}{C} \left. \begin{array}{l} \text{Plot} \\ \text{and} \\ \text{select} \\ \text{good values} \\ \text{for both} \end{array} \right\}$$

select $C = 3.5 \text{ uF} \Rightarrow L = 2.01 \text{ mH}$

$$\omega_c = \pm \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

$$\Rightarrow R \approx 22.74 \text{ } \Omega \text{ for } \omega_{c1} \left. \begin{array}{l} \text{Best} \\ R \text{ found} \\ \text{was } 9.4 \end{array} \right\}$$

$$R \approx 15.34 \text{ } \Omega \text{ for } \omega_{c2}$$

Thus R will likely be
somewhere in that range.

$$2.77 \cdot 10^{-7} = 277 \cdot 10^{-9}$$

$\downarrow R \Rightarrow$ implies tighter corner frequencies

After first iteration,